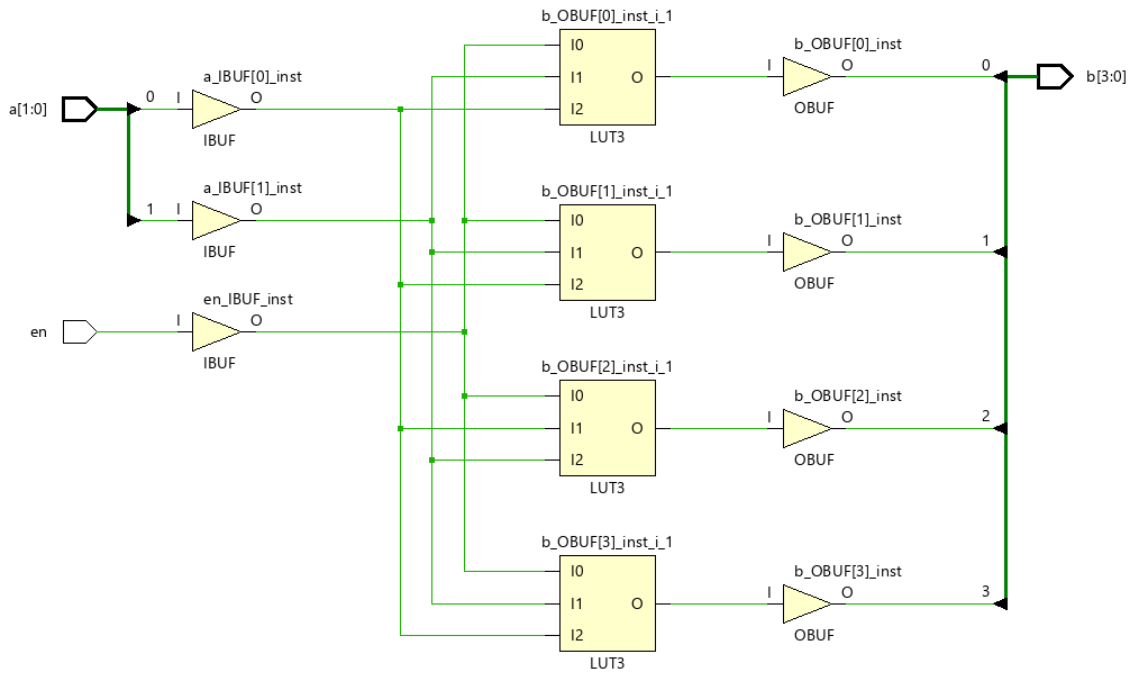



11a)

```
1  -----
2  -- Author: <Cheuk Ki Liu><V00937822>
3  -- Contact info: <cheukkiliu@uvic.ca>
4  --
5  --Acknowledgements: this code is based in part on website
6  --https://www.ece.uvic.ca/~capson/ece441/
7  --
8  -- Module Name: 2-to-4 decoder with an enable signal (en) - Behavioral
9  --
10 -- Description: Assignment#1 question 11 a
11 --
12 -- Course: ECE 441/ ECE543
13 -- Department of Electrical and Computer Engineering
14 -- University of Victoria
15 --
16 -- Date: May 20, 2023
17 --
18 -- Notes: Inputs are 2 bit of a and enable
19 --         Outputs are 4 bit signals: b
20 --         When en is '1', the decoder operates as usual.
21 --         When en is '0', the decoder is disabled and the output is "0000".
22  -----
23
24  library ieee;
25  use ieee.std_logic_1164.all;
26
27  -----
28
29  entity decoder24 is
30
31  port(
32      a: in std_logic_vector(1 downto 0);
33      en: in std_logic ;
34      b: out std_logic_vector (3 downto 0)
35  );
36  end decoder24;
37
38
39  architecture behavioural of decoder24 is
40
41  begin
42      process(a,en)
43
44          begin
45              if ( a="00" and en ='1') then
46                  b <= "0001";
47              elsif ( a="01" and en ='1') then
48                  b <= "0010";
49              elsif ( a="10" and en ='1') then
50                  b <= "0100";
51              elsif ( a="11" and en ='1') then
52                  b <= "1000";
53              else
54                  b <= "0000";
55              end if;
56          end process;
57
58      end behavioural;
59  
```

Synthesis schematics from a Vivado®:




RTL schematics from a Vivado®:

 

11b)

```
1 -----
2 -- Author: <Cheuk Ki Liu><V00937822>
3 -- Contact info: <cheukkiliu@uvic.ca>
4 --
5 --Acknowledgements: this code is based in part on website
6 --https://www.ece.uvic.ca/~capson/ece441/
7 --
8 -- Module Name: 2-to-4 decoder with an enable signal (en) - testbench
9 --
10 -- Description: Assignment#1 question 11 b
11 --
12 -- Course: ECE 441/ ECE543
13 -- Department of Electrical and Computer Engineering
14 -- University of Victoria
15 --
16 -- Date: May 20, 2023
17 --
18 -- Notes: Inputs are 2 bit of a and enable
19 --         Outputs are 4 bit signals: b
20 --         When en is '1', the decoder operates as usual.
21 --         When en is '0', the decoder is disabled and the output is "0000".
22 -----
23
24 library IEEE;
25 use IEEE.STD_LOGIC_1164.ALL;
26 USE IEEE.numeric_std.ALL;
27
28
29 entity decoder24_testbench is
30 end decoder24_testbench;
31
32 architecture simulate of decoder24_testbench is
33
34     signal input_test_pattern: std_logic_vector (2 downto 0);
35
36     signal b: std_logic_vector (3 downto 0);
37
38 begin
39
40 uut : entity work.decoder24 port map(a=>input_test_pattern(1 downto 0), en=>input_test_pattern(2),b => b);
41
42
43
44 process
45 begin
46
47     for i in 0 to 7 loop -- by default, the range 0 to 7 makes "i" an integer
48
49         input_test_pattern <= std_logic_vector(to_unsigned(i, 3));
50         wait for 1 ns;
51
52     end loop;
53
54     -- wait;
55
56 end process;
57
58 end simulate;
```

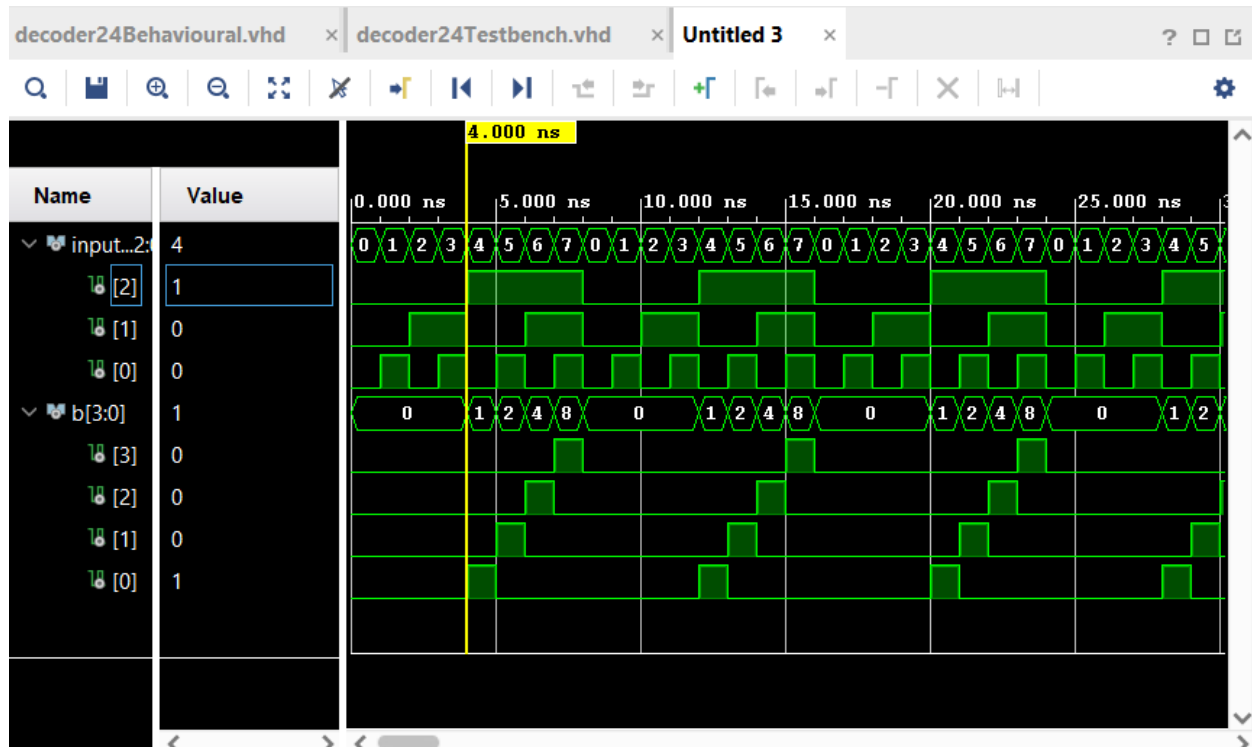

From the timing simulation, when the bit 2 (en) of the input is equal to '0', the output remain 0. When the bit 2 (en) is '1', the decoder operates as usual.

12.

```
1 -----
2 -- Author: <Cheuk Ki Liu><V00937822>
3 -- Contact info: <cheukkiliu@uvic.ca>
4 --
5 --Acknowledgements: this code is based in part on website
6 --https://www.fpga4student.com/2017/06/vhdl-code-for-counters-with-testbench.html
7 --
8 -- Module Name: 4 bit counter - Behavioral
9 --
10 -- Description: Assignment#1 question 12
11 --
12 -- Course: ECE 441/ ECE543
13 -- Department of Electrical and Computer Engineering
14 -- University of Victoria
15 --
16 -- Date: May 20, 2023
17 --
18 -- Notes: Inputs are 2 bit of clock and set/reset
19 --         Outputs are 4 bit signals: q
20 --         4 bit counter counts from 3 ("0011") to 12 ("1100")
21 -----
22
23 library ieee;
24 use ieee.std_logic_1164.all;
25 use IEEE.STD_LOGIC_UNSIGNED.ALL;
26 -----
27
28 entity counter4 is
29
30     port(
31         clk: in std_logic; --clock
32         a: in std_logic ; -- reset
33         q: out std_logic_vector (3 downto 0) --output
34     );
35 end counter4;
36
37
38 architecture behavioural of counter4 is
39     -- make a counter to another variable to save the output value
40     signal count: std_logic_vector (3 downto 0);
41
42 begin
43     process(a,clk)
44     begin
45
46         if ( a = '1') then
47             count <= "0000";
48             -- at the very beginnin
49         elsif (clk'event and clk = '1') then
50             -- rising edge
51             count <= count + "1";
52             if (count < "0011") then
53                 --if count is less then 3
54                 count <= "0011";
55                 --it have to be 3 after next rising edge
56             elsif (count >= "1100") then
57                 --if count is greater then 12
58                 count <= "0011";
59                 --it have to be 3 after next rising edge
60             end if;
61         end if;
62     end process;
63     q <= count;
64 end behavioural;
```

```


1  -----
2  -- Author: <Cheuk Ki Liu><V00937822>
3  -- Contact info: <cheukkiliu@uvic.ca>
4  --
5  --Acknowledgements: this code is based in part on website
6  --https://www.fpga4student.com/2017/06/vhdl-code-for-counters-with-testbench.html
7  --
8  -- Module Name: 4 bit counter - testbench
9  --
10 -- Description: Assignment#1 question 12
11 --
12 -- Course: ECE 441/ ECE543
13 -- Department of Electrical and Computer Engineering
14 -- University of Victoria
15 --
16 -- Date: May 20, 2023
17 --
18 -- Notes: Inputs are 2 bit of clock and set/reset
19 --         Outputs are 4 bit signals: q
20 --         4 bit counter counts from 3 ("0011") to 12 ("1100")
21 -----
22
23
24 library IEEE;
25 use IEEE.STD_LOGIC_1164.ALL;
26 USE IEEE.numeric_std.ALL;
27
28
29 entity counter4_testbench is
30 end counter4_testbench;
31
32 architecture simulate of counter4_testbench is
33
34     signal clk: std_logic;
35     signal a: std_logic;
36     signal q: std_logic_vector (3 downto 0);
37
38 begin
39
40 uut : entity work.counter4 port map(a => a, clk=>clk, q=>q);
41
42 -- start the clock from 0 to 1

```

```

43 clock_start :process
44 begin
45     clk <= '0';
46     wait for 10 ns;
47     clk <= '1';
48     wait for 10 ns;
49 end process;
50
51
52 -- start for simulations
53 stimulation_start: process
54 begin
55
56     -- hold reset state for 20 ns. and start for 420 ns and loop for a cycle
57     a <= '1';
58     wait for 20 ns;
59     a <= '0';
60     wait for 420 ns;
61     a <= '1';
62     wait for 20 ns;
63     a <= '0';
64     wait;
65 end process;
66
67 end simulate;

```

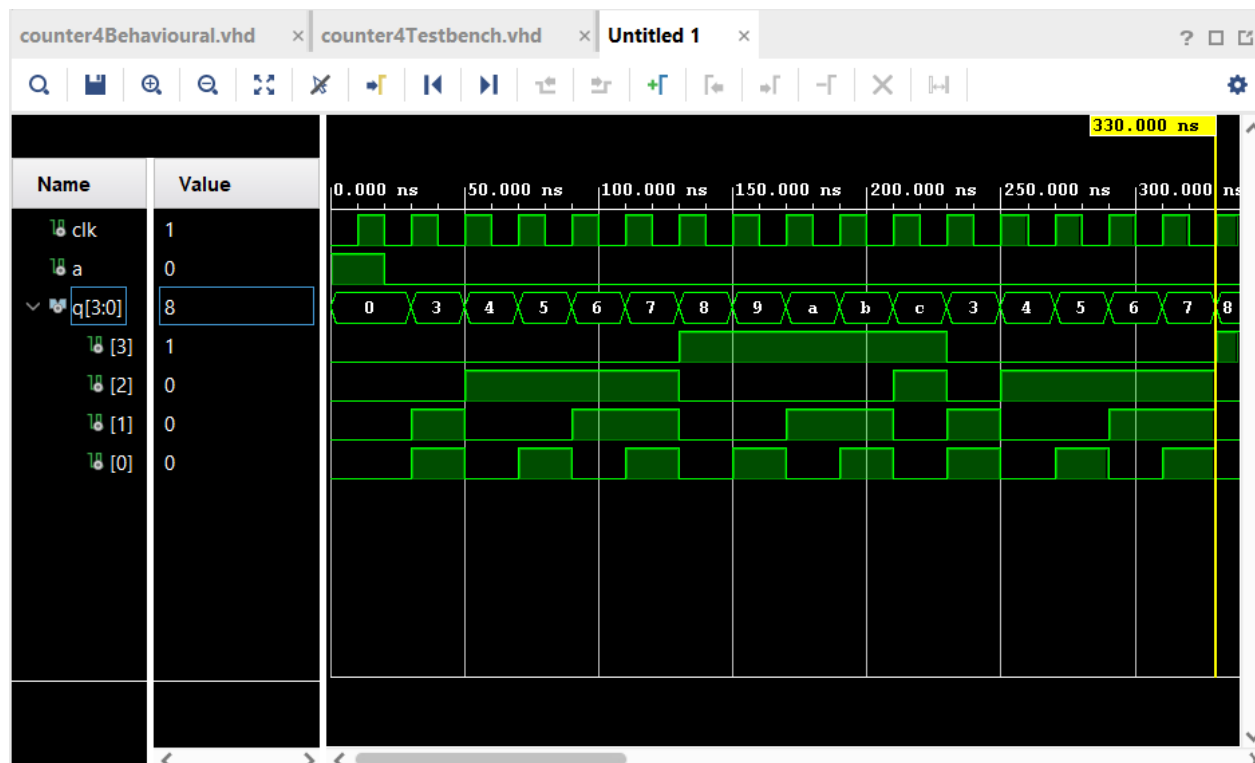

From the time simulation, the 4-bit counter start at 0 and which is the unused state, in the next rising edge of the clock (clk), the output q restart from "0011", then counts from 3 ("0011") to 12 ("1100") and then wraps around.